

ASVAB-SECTION-5^{Q&As}

ASVAB Section Five : Electronic Information

**Pass ASVAB ASVAB-SECTION-5 Exam with 100%
Guarantee**

Free Download Real Questions & Answers **PDF** and **VCE** file from:

<https://www.pass2lead.com/asvab-section-5.html>

100% Passing Guarantee
100% Money Back Assurance

Following Questions and Answers are all new published by ASVAB
Official Exam Center

-  **Instant Download** After Purchase
-  **100% Money Back** Guarantee
-  **365 Days** Free Update
-  **800,000+** Satisfied Customers



QUESTION 1

How many volts does it take to send 99 amps of current through 99,000 ohms of resistance?

- A. 0.009801 volts
- B. 980.1 megavolts
- C. 9.801 megavolts
- D. 98.01 volts

Correct Answer: C

QUESTION 2


A 120 V light bulb is rated for 40 watts. What is the light bulb's current rating?

- A. 3 A
- B. 1/3 A
- C. 2 A
- D. 1 A

Correct Answer: B

$P = IV$, so $I = P/V$ or $I = 40 \text{ Watts}/120 \text{ V} = 1/3 \text{ A}$

QUESTION 3

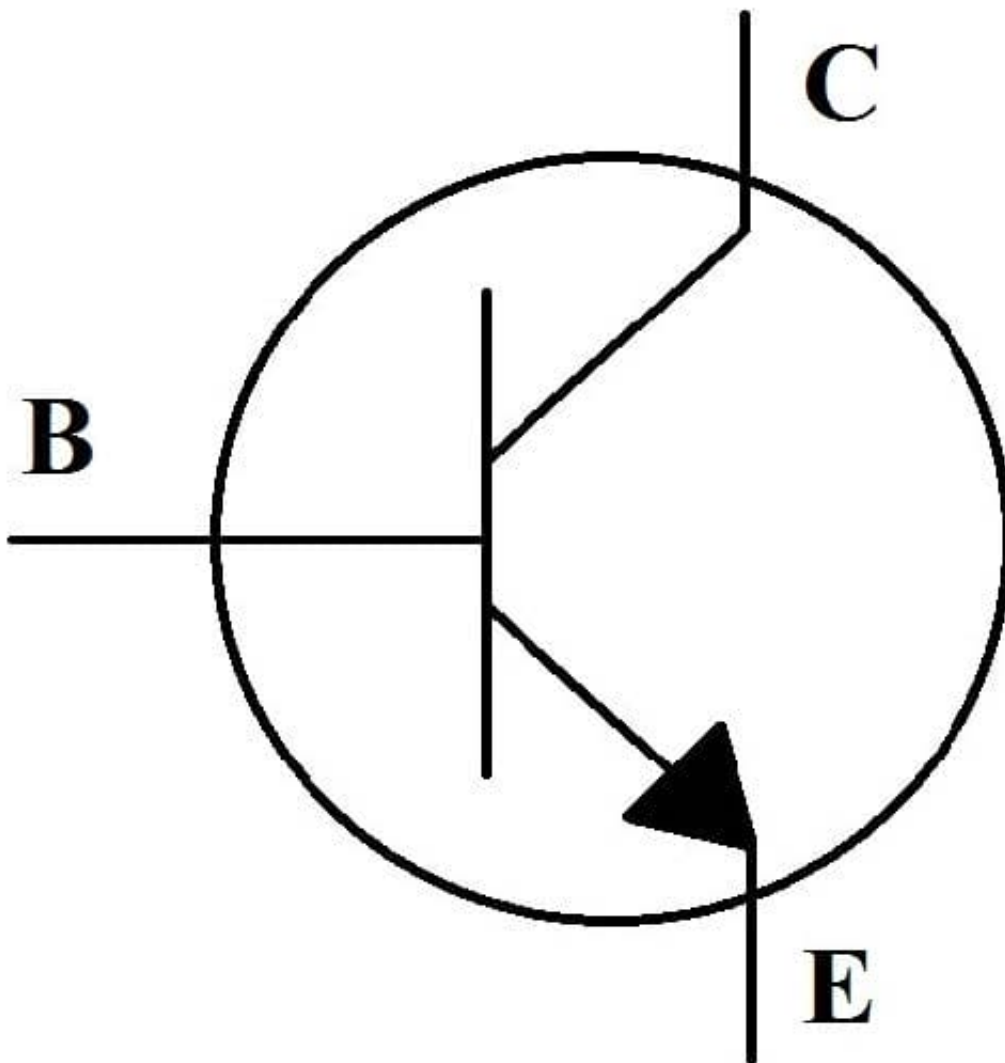

This symbol represents what electronic circuit component?

- A. power source
- B. load
- C. transistor
- D. conductor

Correct Answer: C

QUESTION 4

An oscilloscope is typically used to analyze _____.

- A. resistance
- B. power in a circuit

C. complex waveforms

D. simple circuits

Correct Answer: C

An oscilloscope is used primarily to look at complex waveforms.

QUESTION 5

How many diodes should you expect to find in a bridge rectifier?

A. 0

B. 4

C. 8

D. 10

Correct Answer: C

A bridge rectifier is also known as a full wave rectifier, usually containing 8 diodes.

[Latest ASVAB-SECTION-5
Dumps](#)

[ASVAB-SECTION-5 PDF
Dumps](#)

[ASVAB-SECTION-5
Practice Test](#)