

ASVAB-SECTION-5^{Q&As}

ASVAB Section Five : Electronic Information

**Pass ASVAB ASVAB-SECTION-5 Exam with 100%
Guarantee**

Free Download Real Questions & Answers **PDF** and **VCE** file from:

<https://www.pass2lead.com/asvab-section-5.html>

100% Passing Guarantee
100% Money Back Assurance

Following Questions and Answers are all new published by ASVAB
Official Exam Center

- ⚙️ **Instant Download** After Purchase
- ⚙️ **100% Money Back** Guarantee
- ⚙️ **365 Days** Free Update
- ⚙️ **800,000+** Satisfied Customers



QUESTION 1


To control a light fixture from two different wall switches, you should use _____.

- A. a single-pole switch and a four-way switch
- B. two three-way switches
- C. two four-way switches
- D. two single-pole switches

Correct Answer: B

To control a light fixture from two different positions, use two three-way switches.

QUESTION 2

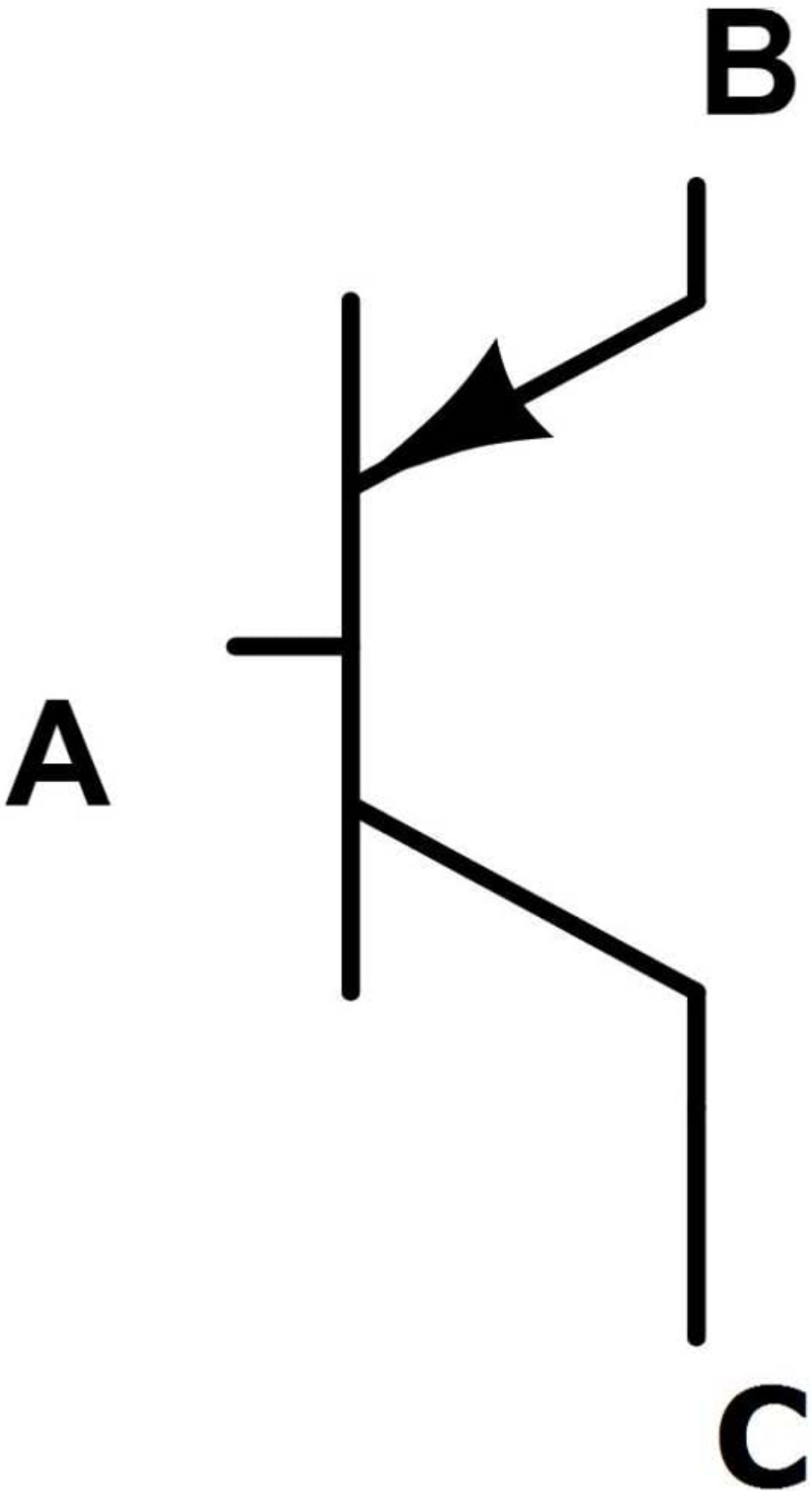

In the diagram of a transistor provided, the letter B corresponds with the _____.

- A. controller
- B. emitter
- C. base
- D. collector

Correct Answer: B

QUESTION 3

How many diodes should you expect to find in a bridge rectifier?

- A. 0
- B. 4
- C. 8
- D. 10

Correct Answer: C

A bridge rectifier is also known as a full wave rectifier, usually containing 8 diodes.

QUESTION 4

Regarding the material found in a transistor, _____ is the name given to the object created by the joining of P-type and N-type material.

- A. semiconductor
- B. integrated circuit
- C. diode
- D. cathode

Correct Answer: C

QUESTION 5

How many volts does it take to send 99 amps of current through 99,000 ohms of resistance?

- A. 0.009801 volts
- B. 980.1 megavolts

C. 9.801 megavolts

D. 98.01 volts

Correct Answer: C

[ASVAB-SECTION-5 PDF
Dumps](#)

[ASVAB-SECTION-5
Practice Test](#)

[ASVAB-SECTION-5
Braindumps](#)